

DIGITAL DESIGN

LAB 4

DIVYAM PATEL


B20EE082

1. Write a Program to implement a
 - a) BCD Adder Unit
 - b) BCD Subtractor Unit

BCD ADDER

Derivation of BCD Adder

Binary Sum					BCD Sum					Decimal
K	Z ₈	Z ₄	Z ₂	Z ₁	C	S ₈	S ₄	S ₂	S ₁	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

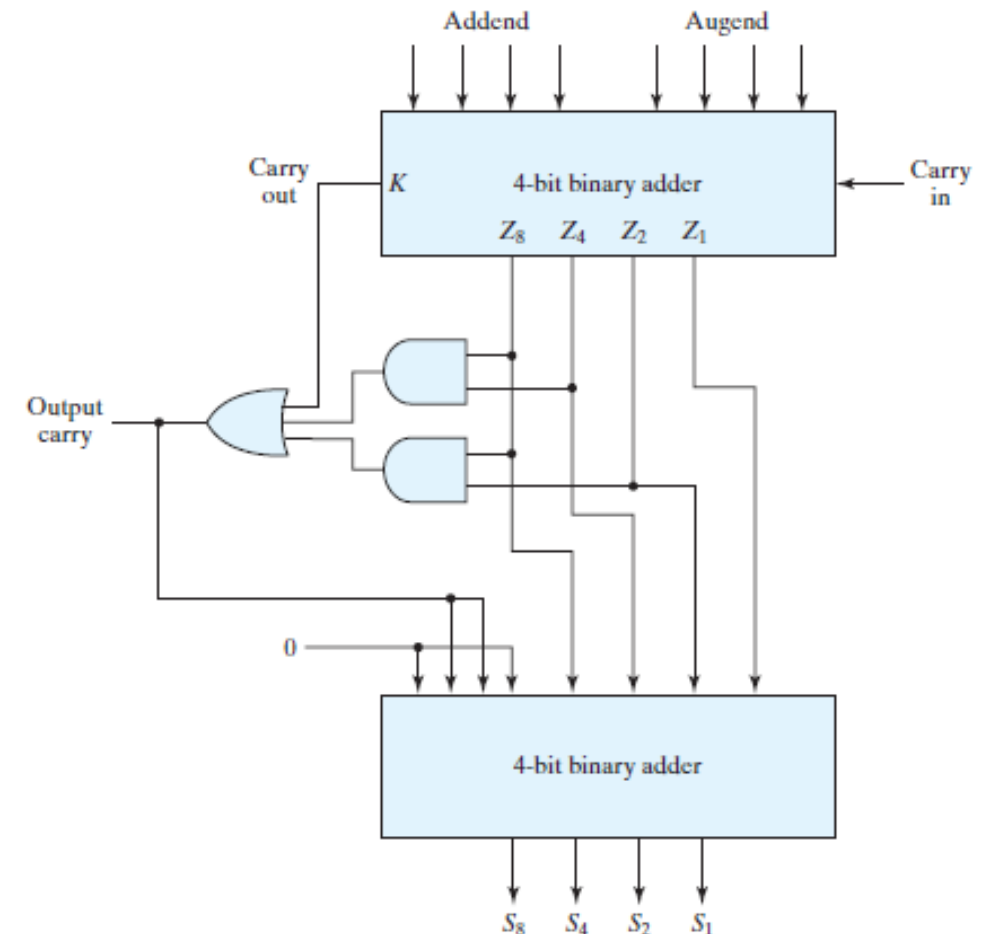


CODE

TESTBENCH

```
1  `timescale 1ns / 1ps
2  //////////////////////////////////////
21
22
23  module test_bcd_adder;
24      reg [3:0] A, B;
25      wire [3:0] S;
26      wire C;
27
28      BCD_adder_unit F1(A, B, S, C);
29
30  initial
31  begin
32      A[3:0] = 4'b0000; B = 4'b0000;
33      #100 A[3:0] = 4'b1001; B = 4'b1001;
34      #100 A[3:0] = 4'b1000; B = 4'b0011;
35      #100 A[3:0] = 4'b1010; B = 4'b0011;
36  end
37  initial #400 $finish;
38  endmodule
```

```
1  `timescale 1ns / 1ps
2  //////////////////////////////////////
21
22
23  module BCD_adder_unit(A, B, S, C);
24      input [3:0] A, B;
25      reg C0 = 1'b0;
26      output [3:0] S;
27      output C;
28
29      wire C1, C2, C3, C4, C5;
30      wire [3:0] X, Z;
31      and (C1, Z[3], Z[2]);
32      and (C2, Z[3], Z[1]);
33      or (C, C3, C1, C2);
34      xor (C5, C, C);
35
36      assign X[2] = C;
37      assign X[1] = C;
38      assign X[3] = C5;
39      assign X[0] = C5;
40      four_bit_adder F_1 (A, B, Z, C3);
41      four_bit_adder F_2 (X, Z, S, C4);
42  endmodule
```

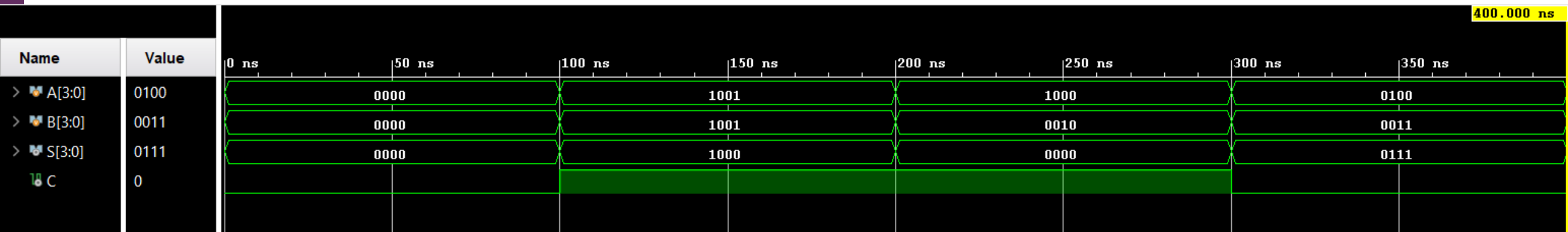

Name	Value
> A[3:0]	0
> B[3:0]	0
> S[3:0]	0
18 C	0

A: 0000, B: 0000,
Sum S: 0000 and
Carry C: 0 for the
BCD adder
(i.e. $0 + 0 = 00$)

Name	Value
> A[3:0]	9
> B[3:0]	9
> S[3:0]	8
18 C	1

A: 1001, B: 1001,
Sum S: 1000 and
Carry C: 1 for the
BCD adder
(i.e. $9 + 9 = 18$)

Name	Value
> A[3:0]	8
> B[3:0]	2
> S[3:0]	0
18 C	1

A: 1000, B: 0010,
Sum S: 0000 and
Carry C: 1 for the
BCD adder
(i.e. $8 + 2 = 10$)

Name	Value
> A[3:0]	4
> B[3:0]	3
> S[3:0]	7
18 C	0

A: 0100, B: 0011,
Sum S: 0111 and
Carry C: 1 for the
BCD adder
(i.e. $4 + 3 = 7$)

BCD SUBTRACTOR

- Find the 10's complement of a negative number
- Add two numbers using BCD addition
- If carry is not generated find the 10s Complement of the result.

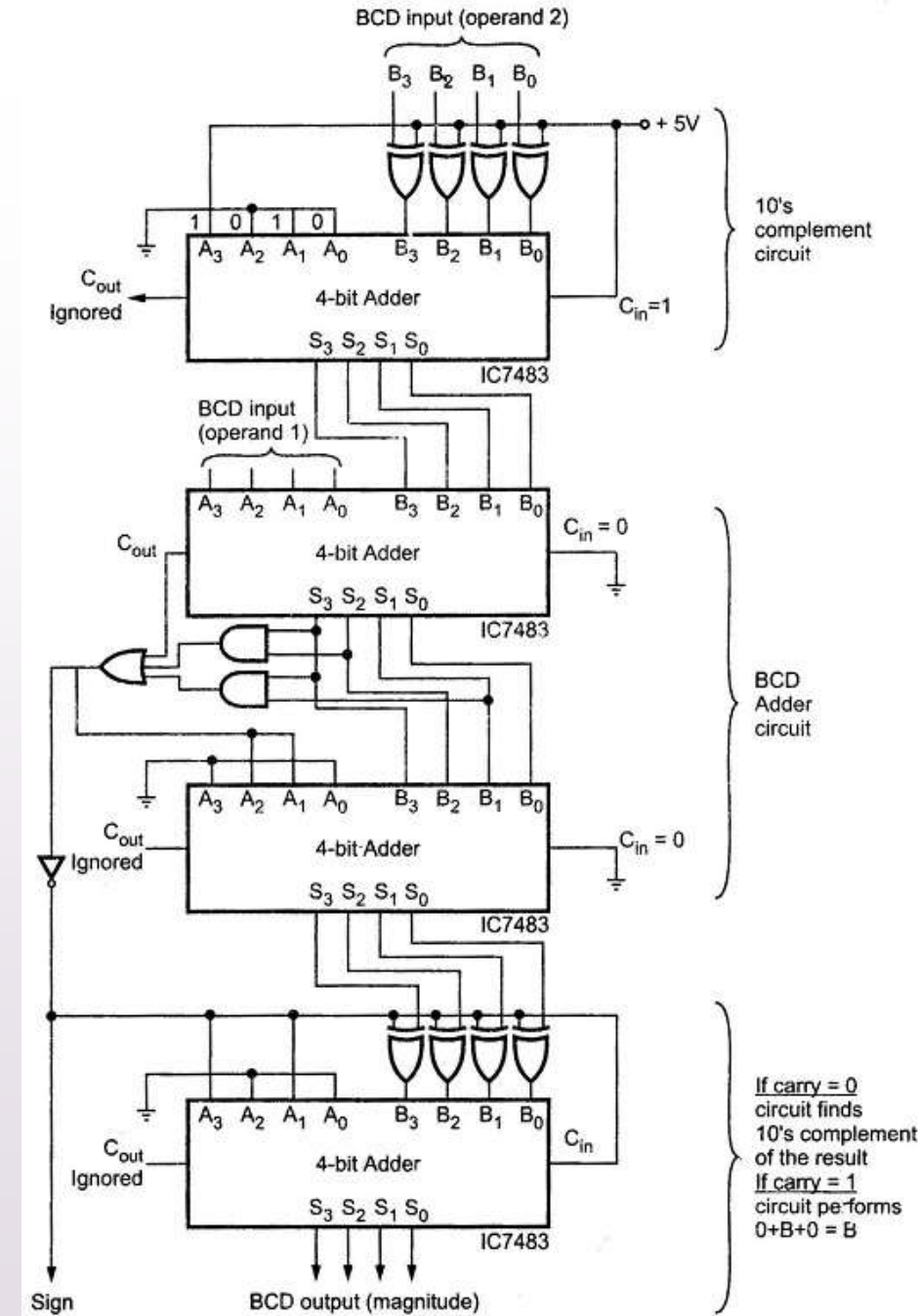



Fig. 3.35 4-bit BCD subtractor using 10's complement method

TESTBENCH

```
1  `timescale 1ns / 1ps
2  //////////////////////////////////////
21
22
23  module test_bcd_subtractor;
24      reg [3:0] A, B;
25      wire [3:0] S;
26      wire C;
27
28      bcd_subtractor_unit F1(A, B, S);
29
30  initial
31  begin
32      A[3:0] = 4'b0000; B = 4'b0000;
33      #100 A[3:0] = 4'b1001; B = 4'b1001;
34      #100 A[3:0] = 4'b1000; B = 4'b0010;
35      #100 A[3:0] = 4'b0100; B = 4'b0011;
36  end
37  initial #400 $finish;
38  endmodule
```

CODE

```
1  `timescale 1ns / 1ps
2  //////////////////////////////////////
21
22  module tens_complement(A,X);
23      input [3:0] A;
24      output [3:0] X;
25
26      assign X[3] = ~(A[3]|A[2]) & ~(A[1]&A[0]);
27      assign X[2] = A[2]^(A[1]&A[0]);
28      assign X[1] = ~(A[1]^A[0]);
29      assign X[0] = A[0];
30  endmodule
31
32  module bcd_subtractor_unit(A,B,S);
33      input [3:0] A,B;
34      output [3:0] S;
35      wire [3:0] B_comp,Z,Z_comp;
36      wire C;
37
38      tens_complement TC1(B,B_comp);
39      BCD_adder_unit BCDA2(A,B_comp,Z,C);
40      tens_complement TC2(Z,Z_comp);
41      assign S = C?Z:Z_comp;
42  endmodule
```

 

Name	Value
> A[3:0]	0000
> B[3:0]	0000
> S[3:0]	0000

Name	Value
> A[3:0]	1001
> B[3:0]	1001
> S[3:0]	0000


Name	Value
> A[3:0]	1000
> B[3:0]	0010
> S[3:0]	0110

Name	Value
> A[3:0]	0100
> B[3:0]	0011
> S[3:0]	0001

Adding A2B0 and A1B1 will give rise to one carry, adding the sum obtained from that, and the carry obtained from adding A1B0 and A0B1 to A0B2 will give rise to another carry. Thus, two carries are generated and are carried over to the addition between A2B1 and A1B2, where two more carries are created similarly. Hence the resulting circuit will contain nine AND gates, three half adders, and three full adders.

CIRCUIT DIAGRAM

3-bit Multiplier

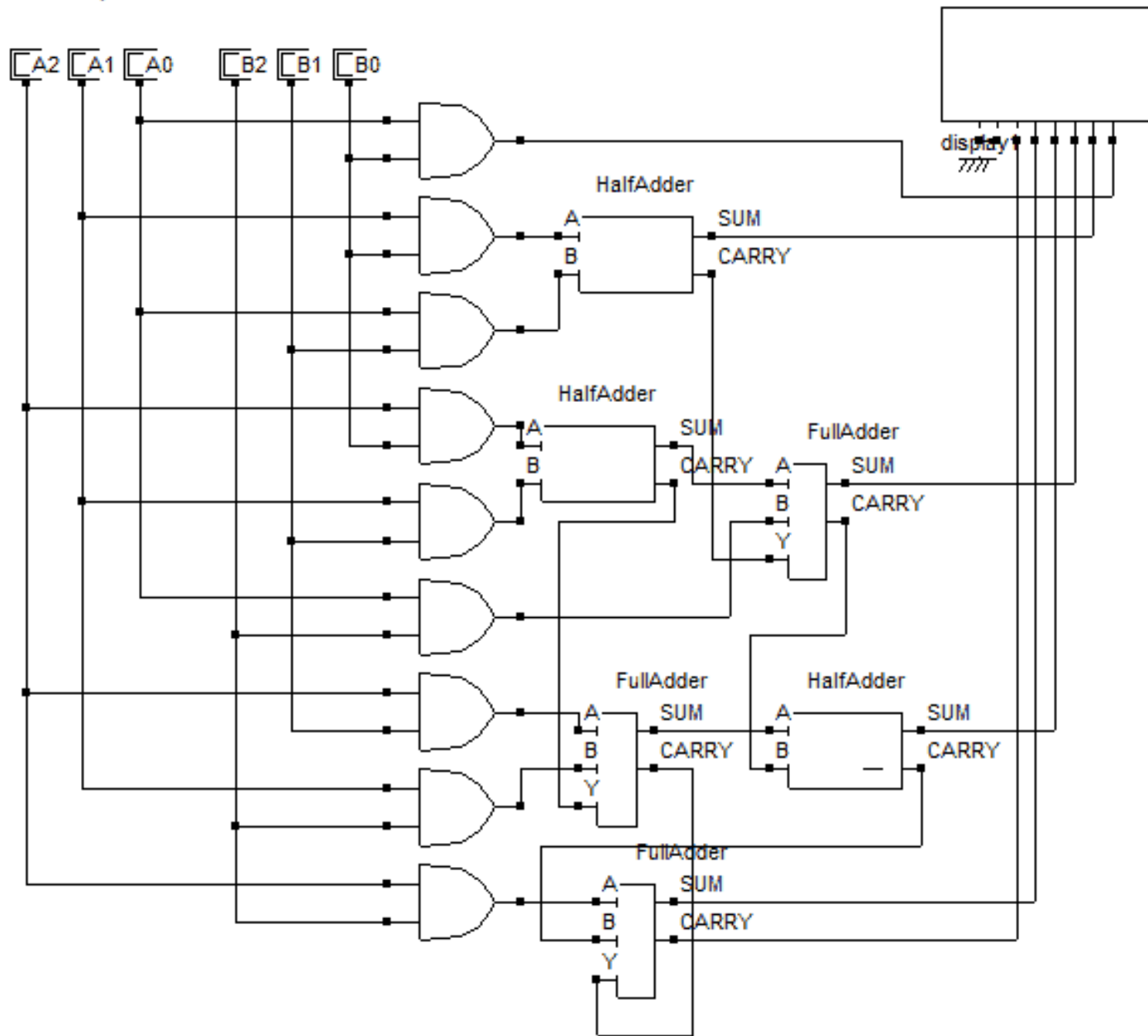

CODE

```
module binary_to_bcd (A,X,Y);
    input [5:0] A;
    output [3:0] X, Y;
    wire [3:0] P, Q, U, V, W;
    wire [2:0] M,N;
    wire O1, O2, C1, Ca, Sa, L, D1, D2, J;
    assign U[3] = A[5] & A[4];
    assign U[2] = ~A[5] & A[4];
    assign U[1] = A[5] ^ A[4];
    assign U[0]=1'b0;

    four_bit_adder FBAA (A[3:0], U, P, C1);
    assign O1 = C1 | (P[3] & (P[2] | P[1]));
    assign V[3] = 1'b0;
    assign V[2] = O1;
    assign V[1] = O1;
    assign V[0] = 1'b0;

    four_bit_adder FBAB (P,V,Q);
    assign O2 = Q[3] & (Q[2] | Q[1]);
    assign W[3] = 1'b0;
    assign W[2] = O2;
    assign W[1] = O2;
    assign W[0] = 1'b0;


    four_bit_adder FBAC(Q,W,X);
    assign N[2] = 1'b0;
    assign N[0] = O1 ^ O2;
    assign N[1] = O1 & O2;
    assign M[0] = A[5] ^ A[4];
    assign J = A[5] & A[4];
    assign M[1] = J ^ A[5];
    assign M[2] = J & A[5];
    assign Y[0] = N[0] ^ M[0];
    assign D1 = M[0]&N[0];
    full_adder FAa (M[1] ,N[1], D1, Y[1], D2);
    full_adder FAb (M[2], N[2], D2, Y[2], Y[3]);
endmodule
```

```
module binary_multiplier(A, B, M, N);
    input [2:0]A,B;
    wire [5:0]q;
    wire [9:1]w;
    output [3:0]M, N;

    and (w[1],A[0],B[0]);
    and (w[2],A[1],B[0]);
    and (w[3],A[0],B[1]);
    and (w[4],A[2],B[0]);
    and (w[5],A[1],B[1]);
    and (w[6],A[0],B[2]);
    and (w[7],A[2],B[1]);
    and (w[8],A[1],B[2]);
    and (w[9],A[2],B[2]);
    wire [4:0]c;
    wire [3:0]s;
    assign q[0] = w[1];
    half_adder F1(w[2],w[3],q[1],c[0]);
    half_adder F2(w[4],w[5],s[0],c[1]);
    full_adder F3(s[0],w[6],c[0],q[2],c[2]);
    full_adder F4(w[7],w[8],c[1],s[1],c[3]);
    half_adder F5(s[1],c[2],q[3],c[4]);
    full_adder F6(w[9],c[4],c[3],q[4],q[5]);
    binary_to_bcd BTB(q, M, N);
endmodule
```

TESTBENCH

```
1  `timescale 1ns / 1ps
2  //////////////////////////////////////
21
22
23  module test_binary_multiplier();
24      reg [2:0]A,B;
25      wire [3:0] tens, ones;
26
27      binary_multiplier BM1(A, B, tens, ones);
28  initial
29  begin
30      A = 3'd4; B = 3'd7;
31      #10 A = 3'd1; B = 3'd6;
32      #10 A = 3'd7; B = 3'd2;
33      #10 A = 3'd6; B = 3'd5;
34      #10 A = 3'd7; B = 3'd7;
35      #10 A = 3'd2; B = 3'd5;
36      #10 A = 3'd6; B = 3'd4;
37      #10 A = 3'd0; B = 3'd3;
38      #10 A = 3'd5; B = 3'd5;
39      #10 A = 3'd3; B = 3'd1;
40  end
41  initial #100 $finish;
42  endmodule
```

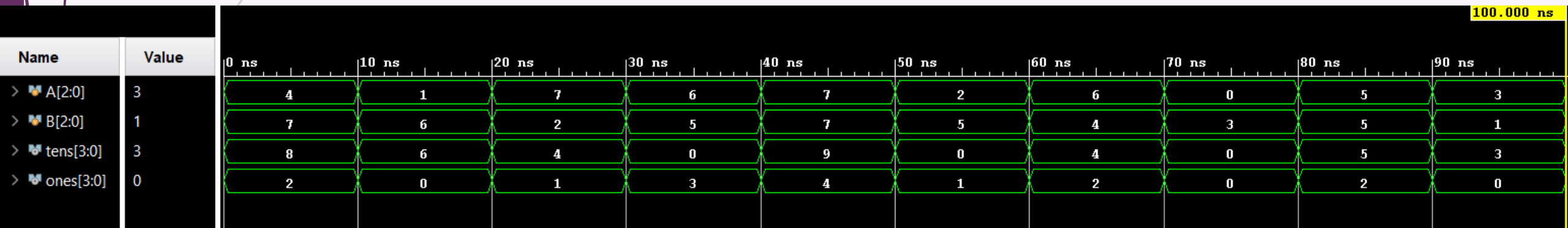

A = 4
B = 7
P = 28

A = 1
B = 6
P = 06

A = 7
B = 2
P = 14

A = 6
B = 5
P = 30

A = 7
B = 7
P = 49

A = 2
B = 5
P = 10

A = 6
B = 4
P = 24

A = 0
B = 3
P = 00

A = 5
B = 5
P = 25

A = 3
B = 1
P = 03



THANK YOU