



# **DIGITAL DESIGN**

## **LAB 6**

**DIVYAM PATEL**

**B20EE082**

# 1. Write a program to implement a D f/f with synchronous and asynchronous reset.

D flip-flop with synchronous reset means the output can reset to zero with the reset input but only with the clock, which makes the reset input dependent on the clock pulse; without clock pulse reset will not be able to set the output Q to zero, which will give us a synchronous output always.

In asynchronous reset the Flip Flop does not wait for the clock and sets the output right at the edge of the reset. In Synchronous Reset, the Flip Flop waits for the next edge of the clock ( rising or falling as designed), before applying the Reset of Data.

# SYNCHRONOUS RESET


## CODE

```
module Synchronous_D(Q,Qbar,D,clock,reset);
    input D,clock,reset;
    output reg Q;
    output Qbar;
    assign Qbar = ~Q;
    always @(posedge clock)
    begin
        if(reset)
            Q<=0;
        else
            Q<=D;
        end
    endmodule
```

## TESTBENCH

```
module test_synchronous();
    reg D,clock,reset;
    wire Q,Qbar;
    Synchronous_D SD(Q,Qbar,D,clock,reset);
    initial
    begin
        clock = 0;
    end
    always
    #100 clock=~clock;
    initial #800 $finish;
    initial
    begin
        clock = 1'b0; D = 1'b0; reset = 1'b0;
        #100 D = 1'b0; reset = 1'b0;
        #100 D = 1'b0; reset = 1'b1;
        #100 D = 1'b0; reset = 1'b1;
        #100 D = 1'b1; reset = 1'b0;
        #100 D = 1'b1; reset = 1'b0;
        #100 D = 1'b1; reset = 1'b1;
        #100 D = 1'b1; reset = 1'b1;
    end
    initial #800 $finish;
endmodule
```

# SIMULATION

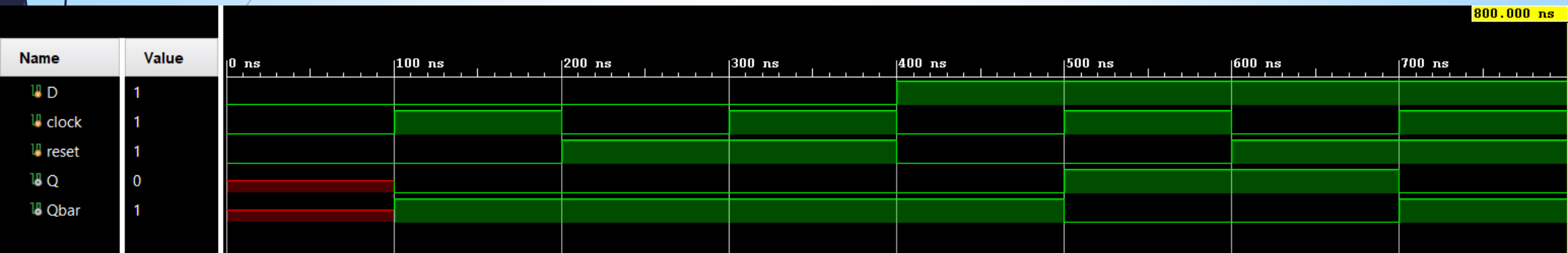

# ASYNCHRONOUS RESET


## CODE

```
module Asynchronous_D(Q,Qbar,clk,D,reset);
    input D,clk,reset;
    output reg Q;
    output Qbar;
    assign Qbar = ~Q;
    always @(posedge clk,posedge reset)
    begin
        if(reset)
            Q<=0;
        else
            Q<=D;
        end
    endmodule
```

## TESTBENCH

```
module test_asynchronous();
    reg clk,D,reset;
    wire Q,Qbar;
    Asynchronous_D AD(Q,Qbar,clk,D,reset);
    initial
    begin
        clk = 1'b0; D = 1'b0; reset = 1'b0;
        #100 D = 1'b0; reset = 1'b0;
        #100 D = 1'b0; reset = 1'b1;
        #100 D = 1'b0; reset = 1'b1;
        #100 D = 1'b1; reset = 1'b0;
        #100 D = 1'b1; reset = 1'b0;
        #100 D = 1'b1; reset = 1'b1;
        #100 D = 1'b1; reset = 1'b1;
    end
    always
    #100 clk = ~clk;
    initial #800 $finish;
endmodule
```

# SIMULATION

 

## 2. Test the operation of blocking and non-blocking assignments using two D flip flops.

### **BLOCKING ASSIGNMENTS :**

Blocking assignment statements are assigned using **=** and are executed one after the other in a procedural block.

However, this will not prevent execution of statements that run in a parallel block.

### **NON-BLOCKING ASSIGNMENTS :**

Non-blocking assignment allows assignments to be scheduled without blocking the execution of following statements and is specified by a **<=** symbol.



# BLOCKING ASSIGNMENT

## CODE


```
module blocking_assignment(D, clock, Q1, Q2);  
input D, clock;  
output reg Q1, Q2;  
always@(posedge clock)  
begin  
    Q1 = D;  
    Q2 = Q1;  
end  
endmodule
```

## TESTBENCH

```
module test_blocking_assignment();  
    reg D, clock;  
    wire Q1, Q2;  
    blocking_assignment bal(D, clock, Q1, Q2);  
    initial  
    begin  
        D=1'b0; clock=1'b0;  
        #10 D=1'b1; clock=1'b0;  
        #10 D=1'b1; clock=1'b1;  
        #10 D=1'b0; clock=1'b1;  
        #10 D=1'b0; clock=1'b0;  
        #10 D=1'b0; clock=1'b1;  
        #10 D=1'b0; clock=1'b0;  
    end  
    initial #80 $finish;  
endmodule
```



# SIMULATION

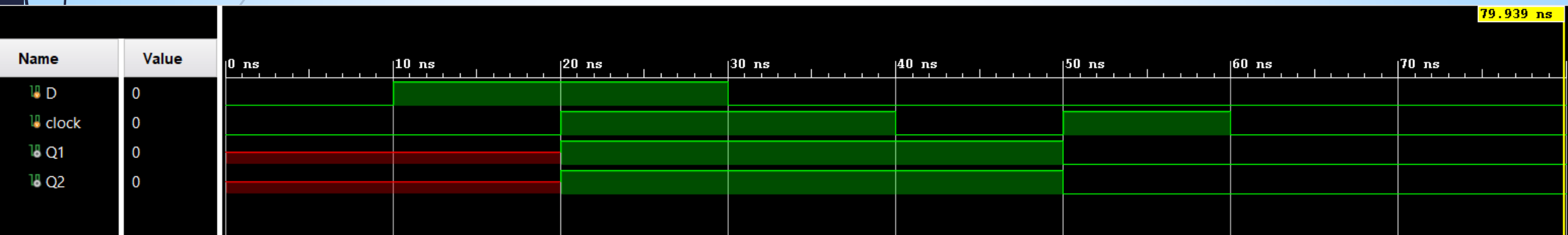

# NON-BLOCKING ASSIGNMENT


## CODE

```
module unblocking_assignment(D, clock, Q1, Q2);
input D, clock;
output reg Q1, Q2;
always@(posedge clock)
begin
    Q1 <= D;
    Q2 <= Q1;
end
endmodule
```

## TESTBENCH

```
module test_nonblocking_assignment();
    reg D, clock;
    wire Q1, Q2;
    unblocking_assignment ual(D, clock, Q1, Q2);
    initial
    begin
        D=1'b0; clock=1'b0;
        #10 D=1'b1; clock=1'b0;
        #10 D=1'b1; clock=1'b1;
        #10 D=1'b0; clock=1'b1;
        #10 D=1'b0; clock=1'b0;
        #10 D=1'b0; clock=1'b1;
        #10 D=1'b0; clock=1'b0;
    end
    initial #80 $finish;
endmodule
```

# SIMULATION

 

**3. Implement the 8 bit serial addition ( $A+B$ ) operation using shift register and a Full Adder. Load the two registers from input using parallel loading. The result should be stored in register A. Find the number of clock cycles your design would take to implement the complete operation.**

Number of clock cycles required : 9  
[1 to load data in SR and 8 for addition]

# CODE

```
module serial_adder(A,B,clk,load,SR1,SR2);
input [7:0]A,B;
input clk,load;
output reg [7:0]SR1,SR2;
wire S,Carry;
reg C=0;
wire [7:0]D,E;

assign D[7]=load?A[7]:SR1[7];
assign D[6]=load?A[6]:SR1[6];
assign D[5]=load?A[5]:SR1[5];
assign D[4]=load?A[4]:SR1[4];
assign D[3]=load?A[3]:SR1[3];
assign D[2]=load?A[2]:SR1[2];
assign D[1]=load?A[1]:SR1[1];
assign D[0]=load?A[0]:SR1[0];

assign E[7]=load?B[7]:SR2[7];
assign E[6]=load?B[6]:SR2[6];
assign E[5]=load?B[5]:SR2[5];
assign E[4]=load?B[4]:SR2[4];
assign E[3]=load?B[3]:SR2[3];
assign E[2]=load?B[2]:SR2[2];
assign E[1]=load?B[1]:SR2[1];
assign E[0]=load?B[0]:SR2[0];
```

```
always @(posedge clk)
begin
if(load)
    SR1[0]=D[0];
    SR1[1]=D[1];
    SR1[2]=D[2];
    SR1[3]=D[3];
    SR1[4]=D[4];
    SR1[5]=D[5];
    SR1[6]=D[6];
    SR1[7]=D[7];


    SR2[0]=E[0];
    SR2[1]=E[1];
    SR2[2]=E[2];
    SR2[3]=E[3];
    SR2[4]=E[4];
    SR2[5]=E[5];
    SR2[6]=E[6];
    SR2[7]=E[7];
end
assign S=SR1[0]^SR2[0]^C;
assign
Carry=(SR1[0]&SR2[0])|(SR2[0]&C)|(C&SR1[0]);
```

```
always @(posedge clk)
begin
if(load==1'b0)
begin
if(Carry==1'bx)
C=0;
else
C=Carry;
SR1[0]=SR1[1];
SR1[1]=SR1[2];
SR1[2]=SR1[3];
SR1[3]=SR1[4];
SR1[4]=SR1[5];
SR1[5]=SR1[6];
SR1[6]=SR1[7];
SR1[7]=S;
SR2[0]=SR2[1];
SR2[1]=SR2[2];
SR2[2]=SR2[3];
SR2[3]=SR2[4];
SR2[4]=SR2[5];
SR2[5]=SR2[6];
SR2[6]=SR2[7];
SR2[7]=S;
end
else
C=0;
end
endmodule
```

# TESTBENCH

```
module test_serial_adder();  
reg [7:0]A,B;  
reg clk,load;  
wire [7:0] SR1,SR2;  
serial_adder SA(A,B,clk,load,SR1,SR2);  
initial  
begin  
    load=0;clk=0;A=8'd45;B=8'd35;#5 load=1;  
    #5 clk=1; #5 load=0;  
    #5 clk=0;  
    #10 clk=1;  
    #10 clk=0;  
    #10 clk=1;  
    #10 clk=0;  
    #10 clk=1;  
    #10 clk=0;A=8'd90;  
    #10 clk=1;  
    #10 clk=0;B=8'd110;  
    #10 clk=1;  
    #10 clk=0;  
    #10 clk=1;  
    #10 clk=0;  
    #10 clk=1;  
    #10 clk=0;  
    #10 clk=1;  
    #10 clk=0;#5load=1;  
    #5 clk=1; #5load=0;  
    #5 clk=0;#10 clk=1;#10 clk=0;#10 clk=1;  
    #10 clk=0;#10 clk=1;#10 clk=0;#10 clk=1;  
    #10 clk=0;#10 clk=1;#10 clk=0;#10 clk=1;  
    #10 clk=0;#10 clk=1;#10 clk=0;#10 clk=1;  
end  
initial #360 $finish;  
endmodule
```

# SIMULATION

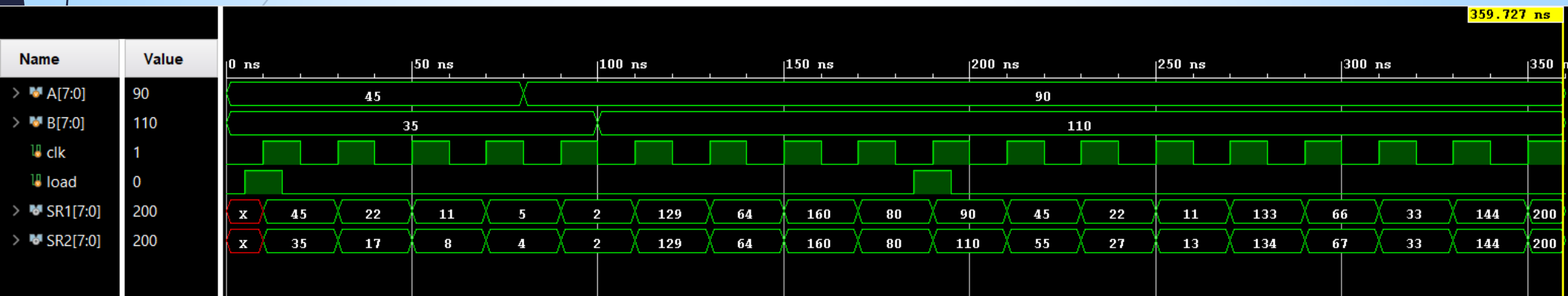





**THANK YOU**