



DIGITAL DESIGN

LAB 5

DIVYAM PATEL

B20EE082


1. Write a program to implement a Barrel Shifter.

TRUTH TABLE

| s_1 | s_0 | y_3 | y_2 | y_1 | y_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | w_3 | w_2 | w_1 | w_0 |
| 0 | 1 | w_0 | w_3 | w_2 | w_1 |
| 1 | 0 | w_1 | w_0 | w_3 | w_2 |
| 1 | 1 | w_2 | w_1 | w_0 | w_3 |

A barrel shifter is a specialized digital electronic circuit with the purpose of shifting an entire data word by a specified number of bits by only using combinational logic, with no sequential logic used.

CIRCUIT DIAGRAM

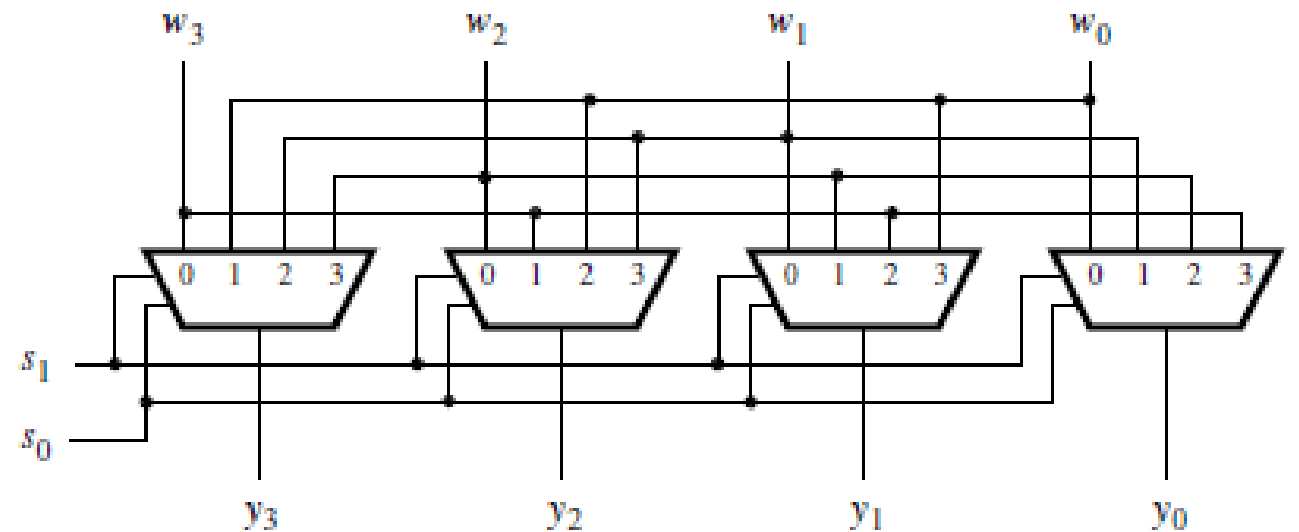


CODE

```
module barrel_shifter(S, W, Y);  
    input [1:0]S;  
    input [3:0]W;  
    output [3:0]Y;  
    wire [3:0] T;  
    assign {T, Y} = {W,W} >> S;  
endmodule
```

TESTBENCH

```
module test_barrel_shifter();  
    reg [1:0]S;  
    reg [3:0]W;  
    wire [3:0]Y;  
  
    barrel_shifter BS(S, W, Y);  
    initial  
        begin;  
            S = 2'b00; W = 4'b0110;  
            #100 S = 2'b01; W = 4'b0110;  
            #100 S = 2'b10; W = 4'b0110;  
            #100 S = 2'b11; W = 4'b0110;  
            #100 S = 2'b00; W = 4'b1011;  
            #100 S = 2'b01; W = 4'b1011;  
            #100 S = 2'b10; W = 4'b1011;  
            #100 S = 2'b11; W = 4'b1011;  
        end  
    initial #800 $finish;  
endmodule
```

SIMULATION

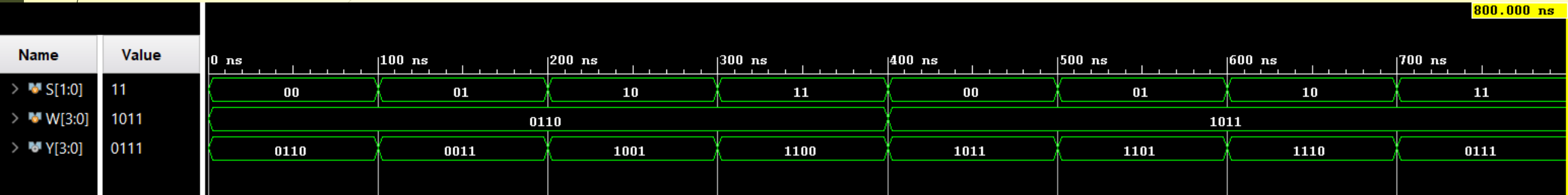

| s1 | s0 | y3 | y2 | y1 | y0 |
|----|----|----|----|----|----|
| 0 | 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 |

| s1 | s0 | y3 | y2 | y1 | y0 |
|----|----|----|----|----|----|
| 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 |

2. Write a Program to implement a 32 bit ALU.

- ALU i.e. Arithmetic Logic Unit is the circuit which can perform both arithmetic as well as logical operations.
- It is basically the calculator of the computer.
- Based on the input we give, it performs the corresponding operation.
- The control unit will supply the data needed by the ALU from memory or from any input devices.

| Operation | Input | 32 bit Output |
|--------------------|-------|---------------|
| Clear | 000 | 0 |
| Addition | 001 | $A + B$ |
| Subtraction | 010 | $A - B$ |
| $A * 2$ | 011 | Left shift |
| $A / 2$ | 100 | Right Shift |
| $A \text{ AND } B$ | 101 | $A \& B$ |
| $A \text{ OR } B$ | 110 | $A B$ |
| $A \text{ XOR } B$ | 111 | $A \wedge B$ |

CODE


 

 
```
module alu_32_bit(S, A, B, Y);
input[2:0] S;
input[31:0] A;
input[31:0] B;
output reg[31:0] Y;
always@(S)
    case(S)
        3'b000: Y = 0; //Clear
        3'b001: Y = A+B; //Addition
        3'b010: Y = A-B; //Subtraction
        3'b011: Y = A<<1; //Left Shift
        3'b100: Y = A>>1; //Right Shift
        3'b101: Y = A&B; //AND
        3'b110: Y = A|B; //OR
        3'b111: Y = A^B; //XOR
    endcase
endmodule
```


TESTBENCH

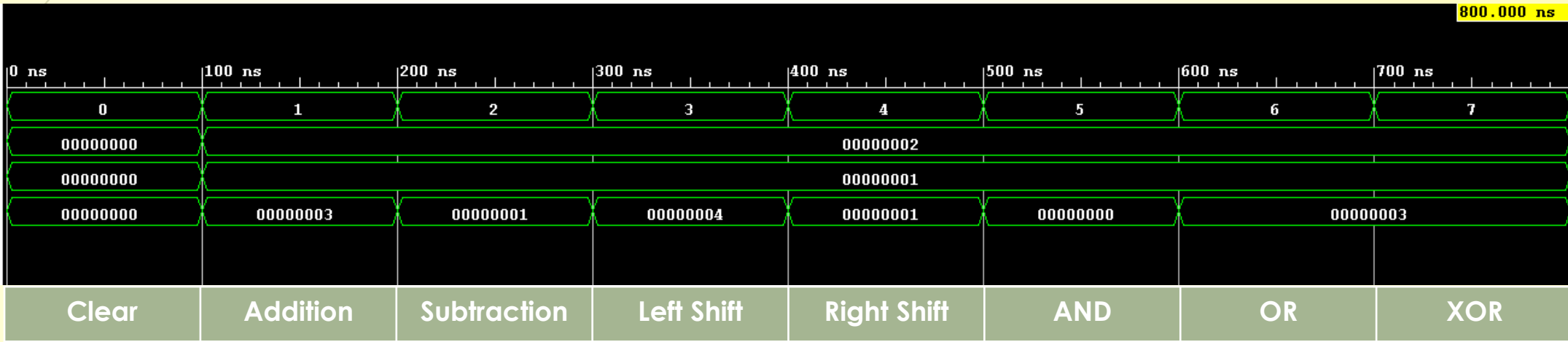
 

 
```
module test_alu_32_bit;
reg [2:0] S;
reg [31:0] A;
reg [31:0] B;
wire [31:0] Y;


alu_32_bit ALU(S, A, B, Y);
initial
begin
    S = 3'b000; A = 2'b00; B = 2'b00;
    #100 S = 3'b001; A = 2'b10; B = 2'b01;
    #100 S = 3'b010; A = 2'b10; B = 2'b01;
    #100 S = 3'b011; A = 2'b10; B = 2'b01;
    #100 S = 3'b100; A = 2'b10; B = 2'b01;
    #100 S = 3'b101; A = 2'b10; B = 2'b01;
    #100 S = 3'b110; A = 2'b10; B = 2'b01;
    #100 S = 3'b111; A = 2'b10; B = 2'b01;
end
initial #800 $finish;
endmodule
```

SIMULATION

| Name | Value |
|---|----------|
| >  S[2:0] | 7 |
| >  A[31:0] | 00000002 |
| >  B[31:0] | 00000001 |
| >  Y[31:0] | 00000003 |



| Name | Value |
|---|----------------------------------|
| >  S[2:0] | 111 |
| >  A[31:0] | 00000000000000000000000000000000 |
| >  B[31:0] | 00000000000000000000000000000000 |
| >  Y[31:0] | 00000000000000000000000000000011 |

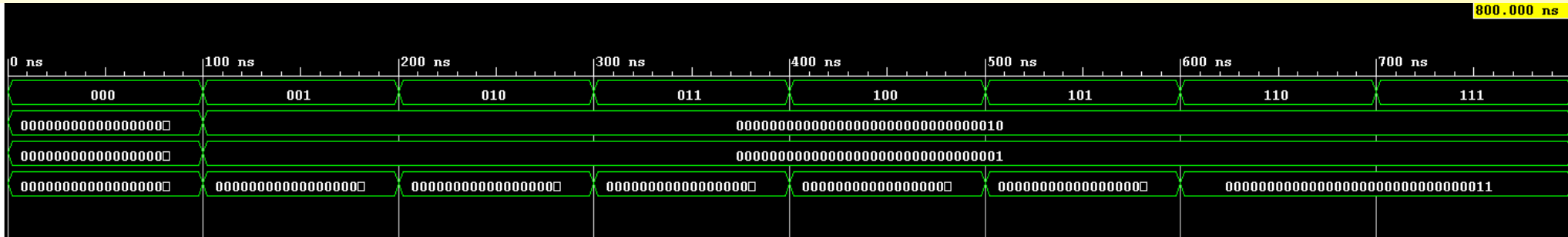

3. Write a program to implement a 4 line to 2 line priority encoder using

a. Casex statements b. For loop

4 to 2 Priority Encoder

This is also referred to as 4- bit priority, which consists of 4 inputs and 2 output lines. Since an encoder contains 2^n input lines and n output lines.

The truth table of a 4 to 2 priority encoder is shown below.

| D3 | D2 | D | D0 | A | B | V |
|----|----|---|----|---|---|---|
| 0 | 0 | 0 | 0 | X | X | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| X | 1 | 0 | 0 | 0 | 1 | 1 |
| X | X | 1 | 0 | 1 | 0 | 1 |
| X | X | X | 1 | 1 | 1 | 1 |

- D3, D2, D1, D0 are the inputs
- A and B are the outputs
- V is the valid bit indicator
- D3 input is the highest priority input
- D0 is the lowest priority input.

4 to 2 Priority Encoder Using Casex Statements

CODE

```
module priority_encoder(A, D, V);
input [3:0]D;
output reg [1:0]A;
output reg V;
always@(D)
begin
V = 1;
    casex(D)
        4'b0001:A = 2'b00;
        4'b001x:A = 2'b01;
        4'b01xx:A = 2'b10;
        4'b1xxx:A = 2'b11;
        default:begin
            V = 0;
            A = 2'bxx;
        end
    endcase
end
endmodule
```

TESTBENCH

```
module test_priority_encoder_casex();
reg [3:0] D;
wire [1:0] A;
wire V;

priority_encoder PEC(A, D, V);
initial
begin
    D = 0;
    #100 D = 4'b0000;
    #100 D = 4'b0001;
    #100 D = 4'b0010;
    #100 D = 4'b0100;
    #100 D = 4'b1000;
end
initial #600 $finish;
endmodule
```

4 to 2 Priority Encoder Using For Loop

CODE


```
module priority_encoder_forloop(A, D, V);
input [3:0]D;
output reg [1:0] A;
output reg V;
integer k;
always @(D)
begin
    A = 2'bxx;
    V = 0;
    for (k = 0; k < 4; k = k+1)
        if (D[k])
            begin
                A = k;
                V = 1;
            end
    end
end
endmodule
```

TESTBENCH


```
module test_priority_encoder_forloop();
reg [3:0] D;
wire [1:0] A;
wire V;

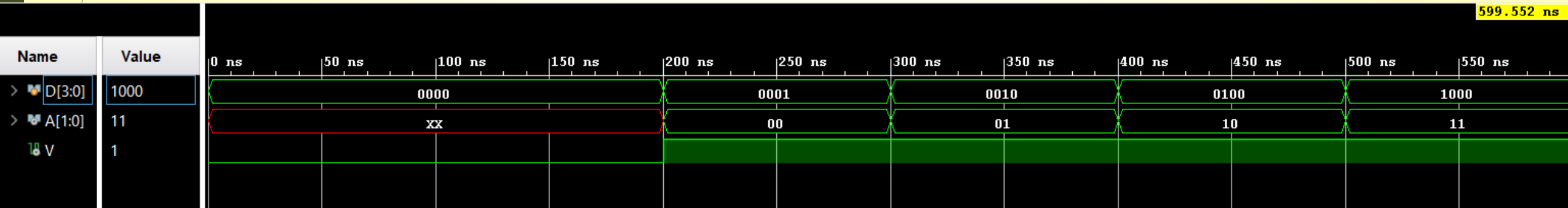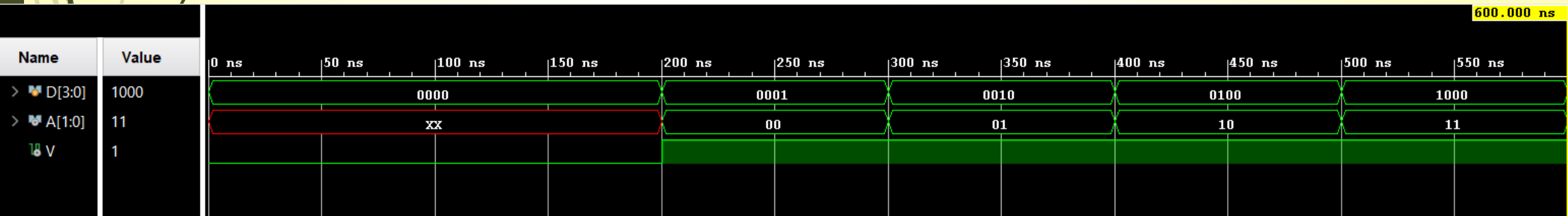
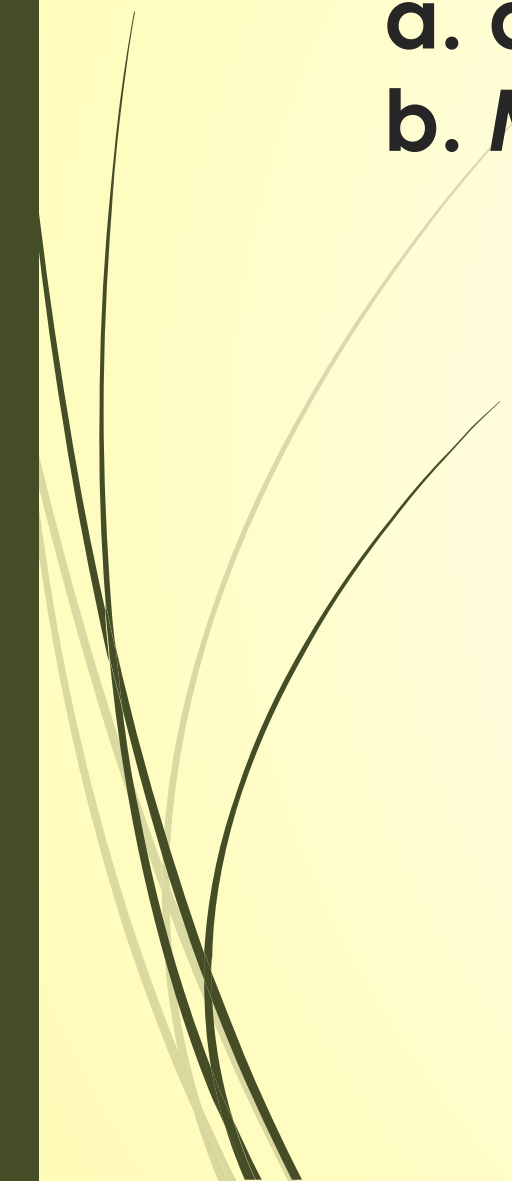
priority_encoder_forloop PEF(A, D, V);
initial
begin
    D = 0;
    #100 D = 4'b0000;
    #100 D = 4'b0001;
    #100 D = 4'b0010;
    #100 D = 4'b0100;
    #100 D = 4'b1000;
end
initial #600 $finish;
endmodule
```

USING CASEX STATEMENTS



USING FOR LOOP



- 
- 
- 4. Write a behavioural code for implementing**
- a. a BCD Adder/Subtractor Unit.**
 - b. Multiply by 5 circuit.**

BCD ADDER

CODE

```
module bcd_adder(A,B,sum,carry);
    input [3:0] A,B;
    output [3:0] sum;
    output reg carry;
    reg [4:0] sum_temp;
    reg [3:0] sum;

    always @(A,B)
    begin
        sum_temp = A+B; //add all the inputs
        if(sum_temp > 9)
            begin
                sum_temp = sum_temp+6; //add 6, if result is more than 9.
                carry = 1; //set the carry output
                sum = sum_temp[3:0];
            end
        else
            begin
                carry = 0;
                sum = sum_temp[3:0];
            end
        end
    end
endmodule
```



TESTBENCH

```
module test_bcd_adder();
    reg [3:0] A;
    reg [3:0] B;
    wire [3:0] sum;
    wire carry;

    bcd_adder BA1(A,B,sum,carry);

    initial begin
        A = 0; B = 0; #100;
        A = 6; B = 9; #100;
        A = 3; B = 3; #100;
        A = 4; B = 5; #100;
        A = 8; B = 2; #100;
        A = 9; B = 9; #100;
    end
    initial #700 $finish;
endmodule
```

SIMULATION

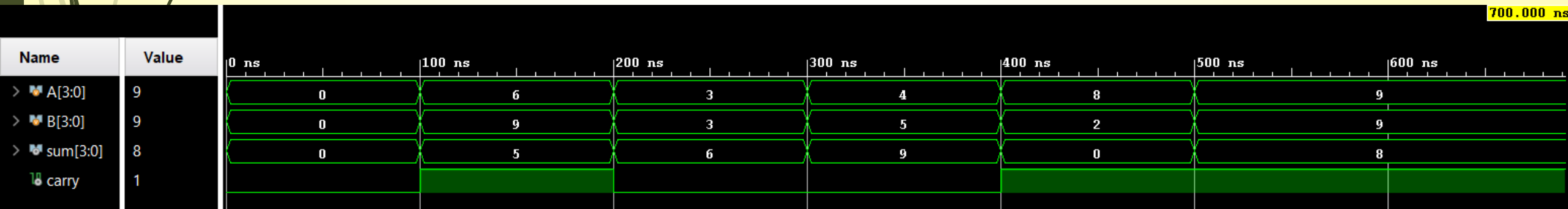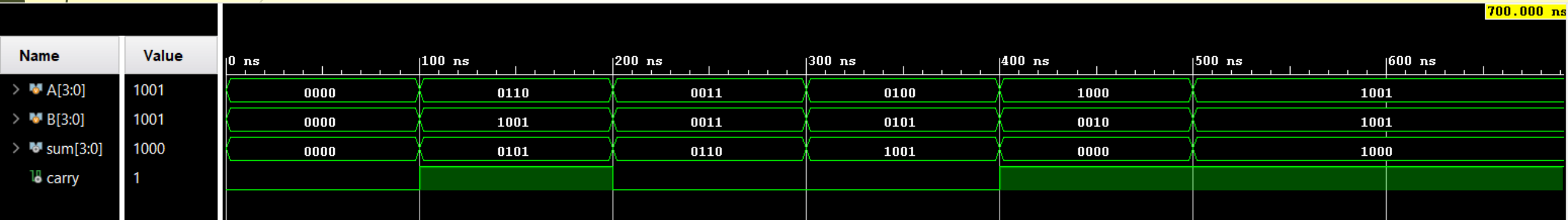

BCD SUBTRACTOR

CODE

```
module bcd_subtractor(A,B,s,cout);
    input [3:0] A,B;
    output reg[3:0] s;
    output reg cout;

    always @(A,B)
    begin
        if (A>B)
            begin
                s = A - B;
                cout = 0;
            end
        else if (A<B)
            begin
                s = B - A;
                cout = 1;
            end
        else
            begin
                s = 0;
                cout = 0;
            end
        end
    end
endmodule
```

TESTBENCH

```
module test_add_sub();
    reg [3:0] A, B;
    wire [3:0] s;
    wire cout;

    bcd_subtractor BS(A,B,s,cout);
    initial
        begin
            A = 0;   B = 0;   #100;
            A = 6;   B = 9;   #100;
            A = 5;   B = 3;   #100;
            A = 4;   B = 5;   #100;
            A = 8;   B = 2;   #100;
            A = 9;   B = 9;   #100;
        end
    initial #700 $finish;
endmodule
```

SIMULATION

| | | 694.171 ns | | | | | | |
|----------|-------|------------|--------|--------|--------|--------|--------|--------|
| Name | Value | 0 ns | 100 ns | 200 ns | 300 ns | 400 ns | 500 ns | 600 ns |
| > A[3:0] | 1001 | 0000 | 0110 | 0101 | 0100 | 1000 | | 1001 |
| > B[3:0] | 1001 | 0000 | 1001 | 0011 | 0101 | 0010 | | 1001 |
| > s[3:0] | 0000 | 0000 | 0011 | 0010 | 0001 | 0110 | | 0000 |
| cout | 0 | | | | | | | |

| | | 694.171 ns | | | | | | |
|----------|-------|------------|--------|--------|--------|--------|--------|--------|
| Name | Value | 0 ns | 100 ns | 200 ns | 300 ns | 400 ns | 500 ns | 600 ns |
| > A[3:0] | 9 | 0 | 6 | 5 | 4 | 8 | | 9 |
| > B[3:0] | 9 | 0 | 9 | 3 | 5 | 2 | | 9 |
| > s[3:0] | 0 | 0 | 3 | 2 | 1 | 6 | | 0 |
| cout | 0 | | | | | | | |

MULTIPLY BY 5


CODE

```
module multiply_5(I, O);  
  input [3:0] I;  
  output [5:0] O;  
  assign O = (I<<2) + I;  
endmodule
```

TESTBENCH

```
module test_multiply_5();  
  reg [3:0] I;  
  wire [5:0] O;  
  multiply_5 M1(I, O);  
  initial  
    begin  
      I = 4'b0010; #100;  
      I = 4'b1000; #100;  
      I = 4'b1100; #100;  
      I = 4'b0111; #100;  
      I = 4'b1011; #100;  
      I = 4'b1100; #100;  
    end  
  initial #700 $finish;  
endmodule
```

SIMULATION

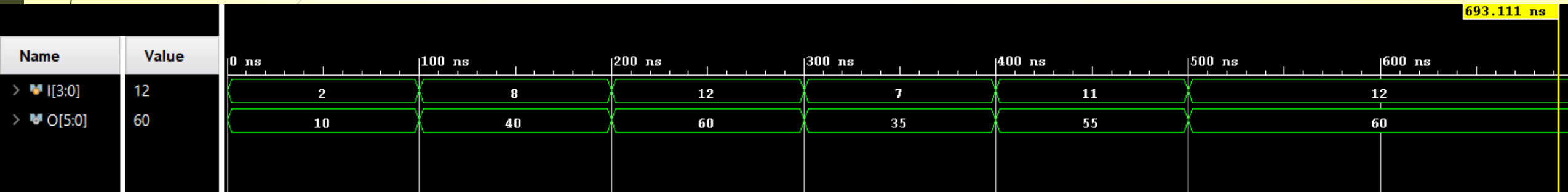

Output is multiplied by 5



THANK YOU