



# **DIGITAL DESIGN**

## **LAB 8**


**DIVYAM PATEL**

**B20EE082**

# 1. Create the 8bit MLS counter using LFSR.

## CODE

### 8 BIT LFSR

 

```
module mls_counter(A,reset,clk,O);  
input [1:8] A;  
input reset,clk;  
output O;  
reg [1:8] X;  
wire V;
```


```
always @(posedge reset)  
begin  
X[1]<=A[1];  
X[2]<=A[2];  
X[3]<=A[3];  
X[4]<=A[4];  
X[5]<=A[5];  
X[6]<=A[6];  
X[7]<=A[7];  
X[8]<=A[8];  
end
```

```
always @(posedge clk)  
begin  
X[1]<=V;  
X[2]<=X[1];  
X[3]<=X[2];  
X[4]<=X[3];  
X[5]<=X[4];  
X[6]<=X[5];  
X[7]<=X[6];  
X[8]<=X[7];  
end
```

```
assign V=X[8]^X[6]^X[5]^X[4];  
assign O=X[8];  
endmodule
```

```
module test_mls();  
    reg [1:8] A;  
    reg reset, clk;  
    wire O;  
  
    mls_counter MLS(A, reset, clk, O);  
  
initial  
begin  
    A=8'b10101011; reset=0; clk=0;  
    #5 reset=1; #1 reset=0; #4 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
    #10 clk=0; #10 clk=1;  
end  
initial #400 $finish;  
endmodule
```

# SIMULATION

 



**2. Write a program to implement 2's complement of a running bitstream using**

**a) Melay Machine**

**b) Moore Machine**

**Use LFSR for generating input bitstream.**



# CODE

```
module melay(X,load,ctrl,clk,Y);
input [3:0]X;
input load,ctrl,clk;
output reg [3:0] Y;
wire D,V;
reg A=0;

always @(posedge clk)
begin
    if(load)
    begin
        Y[0]=X[0];
        Y[1]=X[1];
        Y[2]=X[2];
        Y[3]=X[3];
    end
    if(ctrl)
    begin
        A<=D;
        Y[0]<=Y[1];
        Y[1]<=Y[2];
        Y[2]<=Y[3];
        Y[3]<=V;
    end
end

assign D= A | Y[0];
assign V= Y[0]^A;
endmodule
```


# MELAY MACHINE

## TESTBENCH

```
module test_melay();
reg [3:0] X;
reg load,ctrl,clk;
wire [3:0] Y;
melay me(X,load,ctrl,clk,Y);

initial
begin
    X=4'b0111; load =0; ctrl=0; clk=0;
    #5 load=1;
    #5 clk=1; #5 load=0;
    #5 clk=0; #5 ctrl=1;
    #5 clk=1;
    #10 clk=0;
    #10 clk=1;
    #10 clk=0;
    #10 clk=1;
    #10 clk=0;
    #10 clk=1; #5 ctrl=0;
end
initial #100 $finish;
endmodule
```

# SIMULATION

 

# CODE

```
module moore(X,load,ctrl,clk,Y);
input [3:0]X;
input load,ctrl,clk;
output reg [3:0] Y;
wire D1,D2;
reg A=0,B=0;

always @(posedge clk)
begin
    if(load)
    begin
        Y[0]=X[0];
        Y[1]=X[1];
        Y[2]=X[2];
        Y[3]=X[3];
    end

    if(ctrl)
    begin
        A<=D1;
        B<=D2;
        Y[0]<=Y[1];
        Y[1]<=Y[2];
        Y[2]<=Y[3];
        Y[3]<=B;
    end
end

assign D1=Y[0] & (A | B);
assign D2=Y[0] ^ (A | B);
endmodule
```

# MOORE MACHINE

## TESTBENCH


```
module test_moore();
reg [3:0] X;
reg load,ctrl,clk;
wire [3:0] Y;
moore mo(X,load,ctrl,clk,Y);

initial
begin
    X=4'd8; load =0; ctrl=0; clk=0;
    #5 load=1;
    #5 clk=1; #5 load=0;
    #5 clk=0; #5 ctrl=1;
    #5 clk=1;
    #10 clk=0;
    #10 clk=1;
    #10 clk=0;
    #10 clk=1;
    #10 clk=0;
    #10 clk=1;
    #10 clk=0;
    #10 clk=1; #5 ctrl=0;
end

initial #120 $finish;
endmodule
```



# SIMULATION

 



**THANK YOU**