



# **DIGITAL DESIGN**

## **LAB 2**


**DIVYAM PATEL**

**B20EE082**

# Work 1: BINARY TO GRAY CODE CONVERTER

BINARY TO GRAY CODE CONVERTER TRUTH TABLE

INPUT				OUTPUT			
B4	B3	B2	B1	G4	G3	G2	G1
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

 

# CODE

```
Project Summary x binary_to_gray.v x test_binary_to_gray.v x
D:/YEAR 2/SEMESTER 2/DIGITAL DESIGN/LABS/LAB 2/binary_to_gray.v

1  `timescale 1ns / 1ps
2  ////////////////////////////////////////...
21
22
23  module binary_to_gray(B,G);
24      input [4:1]B;      // binary input
25      output [4:1]G;     // gray code output
26
27      assign G[4] = B[4];
28      assign G[3] = B[4] ^ B[3];
29      assign G[2] = B[3] ^ B[2];
30      assign G[1] = B[2] ^ B[1];
31
32  endmodule
```

```
module binary_to_gray(B,G);
input [4:1]B;    // binary input
output [4:1]G;   // gray code output
```

```
assign G[4] = B[4];
assign G[3] = B[4] ^ B[3];
assign G[2] = B[3] ^ B[2];
assign G[1] = B[2] ^ B[1];
```

```
endmodule
```

D:/YEAR 2/SEMESTER 2/DIGITAL DESIGN/LABS/LAB 2/test\_binary\_to\_gray.v



```

19 //
20 //////////////////////////////////////////////////
21
22
23 module test_binary_to_gray;
24     reg [4:1]B;
25     wire [4:1]G;
26     binary_to_gray G1(B,G);
27
28     initial
29     begin
30         B = 4'b0000;
31         #10 B = 4'b0001;
32         #10 B = 4'b0010;
33         #10 B = 4'b0011;
34         #10 B = 4'b0100;
35         #10 B = 4'b0101;
36         #10 B = 4'b0110;
37         #10 B = 4'b0111;
38         #10 B = 4'b1000;
39         #10 B = 4'b1001;
40         #10 B = 4'b1010;
41         #10 B = 4'b1011;
42         #10 B = 4'b1100;
43         #10 B = 4'b1101;
44         #10 B = 4'b1110;
45         #10 B = 4'b1111;
46     end
47
48     initial #160 $finish;
49 endmodule

```

## TEST BENCH

```

module test_binary_to_gray;
reg [4:1]B;
wire [4:1]G;
binary_to_gray G1(B,G);

```

```

initial
begin
B = 4'b0000;
#10 B = 4'b0001;
#10 B = 4'b0010;
#10 B = 4'b0011;
#10 B = 4'b0100;
#10 B = 4'b0101;
#10 B = 4'b0110;
#10 B = 4'b0111;
#10 B = 4'b1000;
#10 B = 4'b1001;
#10 B = 4'b1010;
#10 B = 4'b1011;
#10 B = 4'b1100;
#10 B = 4'b1101;
#10 B = 4'b1110;
#10 B = 4'b1111;

```

```

#10 B = 4'b1000;
#10 B = 4'b1001;
#10 B = 4'b1010;
#10 B = 4'b1011;
#10 B = 4'b1100;
#10 B = 4'b1101;
#10 B = 4'b1110;
#10 B = 4'b1111;
end


```

```


initial #160 $finish;
endmodule

```

# SIMULATION

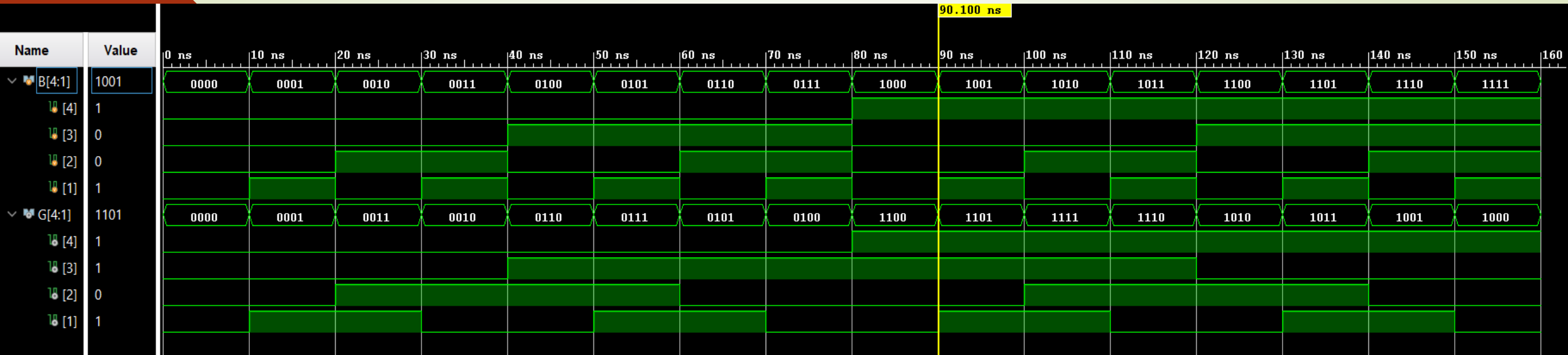

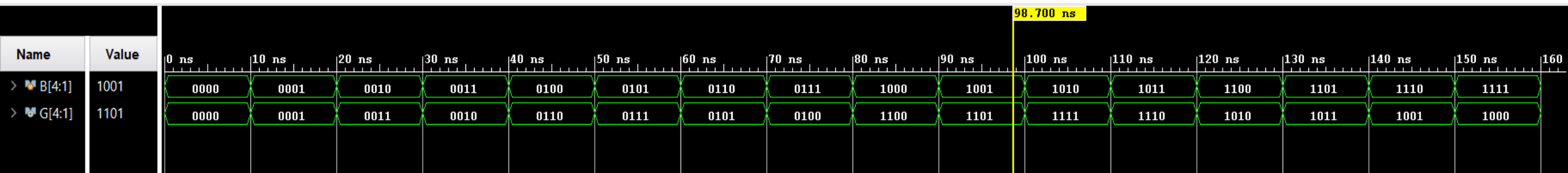
test\_binary\_to\_gray.v × binary\_to\_gray.v × Untitled 2 × ?



# Work 1: GRAY TO BINARY CODE CONVERTER

GRAY TO BINARY CODE CONVERTER TRUTH TABLE

INPUT				OUTPUT			
G4	G3	G2	G1	B4	B3	B2	B1
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	1	0	0	1	0
0	0	1	0	0	0	1	1
0	1	1	0	1	1	0	0
0	1	1	1	1	1	0	1
0	1	0	1	1	1	1	0
0	1	0	0	1	1	1	1
1	1	0	0	0	1	0	0
1	1	0	1	0	1	0	1
1	1	1	1	0	1	1	0
1	1	1	0	0	1	1	1
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	1
1	0	0	1	1	0	1	0
1	0	0	0	1	0	1	1

 

## CODE

D:/YEAR 2/SEMESTER 2/DIGITAL DESIGN/LABS/LAB 2/gray\_to\_binary.v



```
1  `timescale 1ns / 1ps
2  //////////////////////////////////////
21
22
23  module gray_to_binary(G,B);
24      input  [4:1]G;      // gray code input
25      output [4:1]B;      // binary output
26
27      assign B[4] = G[4];
28      assign B[3] = G[4] ^ G[3];
29      assign B[2] = G[4] ^ G[3] ^ G[2];
30      assign B[1] = G[4] ^ G[3] ^ G[2] ^ G[1];
31
32  endmodule
```

```
module gray_to_binary(G,B);
input [4:1]G;    // gray code input
output [4:1]B;  // binary output
```

```
assign B[4] = G[4];
assign B[3] = G[4] ^ G[3];
assign B[2] = G[4] ^ G[3] ^ G[2];
assign B[1] = G[4] ^ G[3] ^ G[2] ^ G[1];
```

```
endmodule
```

D:/YEAR 2/SEMESTER 2/DIGITAL DESIGN/LABS/LAB 2/test\_gray\_to\_binary.v



```

1  `timescale 1ns / 1ps
2  //////////////////////////////////////
21
22
23 module test_gray_to_binary;
24     reg [4:1]G;
25     wire [4:1]B;
26     gray_to_binary B1(G,B);
27
28     initial
29     begin
30         G = 4'b0000;
31         #10 G = 4'b0001;
32         #10 G = 4'b0011;
33         #10 G = 4'b0010;
34         #10 G = 4'b0110;
35         #10 G = 4'b0111;
36         #10 G = 4'b0101;
37         #10 G = 4'b0100;
38         #10 G = 4'b1100;
39         #10 G = 4'b1101;
40         #10 G = 4'b1111;
41         #10 G = 4'b1110;
42         #10 G = 4'b1010;
43         #10 G = 4'b1011;
44         #10 G = 4'b1001;
45         #10 G = 4'b1000;
46     end
47
48     initial #160 $finish;
49 endmodule

```

## TEST BENCH

```

module test_gray_to_binary;
reg [4:1]G;
wire [4:1]B;
gray_to_binary B1(G,B);

```

```

initial
begin
G = 4'b0000;
#10 G = 4'b0001;
#10 G = 4'b0011;
#10 G = 4'b0010;
#10 G = 4'b0110;
#10 G = 4'b0111;
#10 G = 4'b0101;
#10 G = 4'b0100;
#10 G = 4'b1100;
#10 G = 4'b1101;
#10 G = 4'b1111;
#10 G = 4'b1110;
#10 G = 4'b1010;
#10 G = 4'b1011;
#10 G = 4'b1001;
#10 G = 4'b1000;

```

```

#10 G = 4'b1100;
#10 G = 4'b1101;
#10 G = 4'b1111;
#10 G = 4'b1110;
#10 G = 4'b1010;
#10 G = 4'b1011;
#10 G = 4'b1001;
#10 G = 4'b1000;
end

```



```

initial #160 $finish;
endmodule


```



## SIMULATION

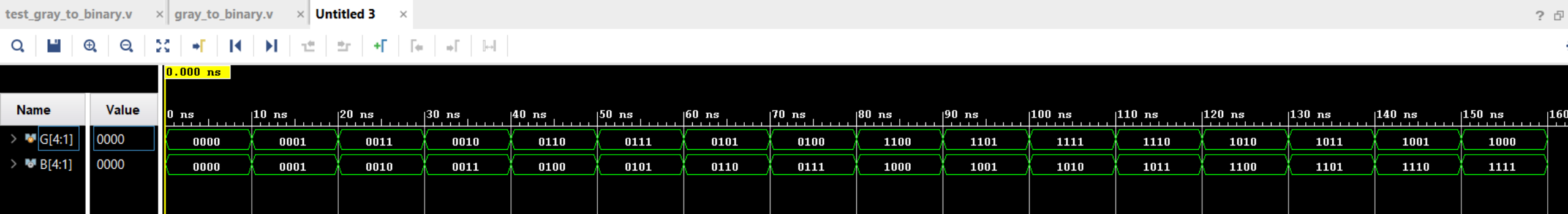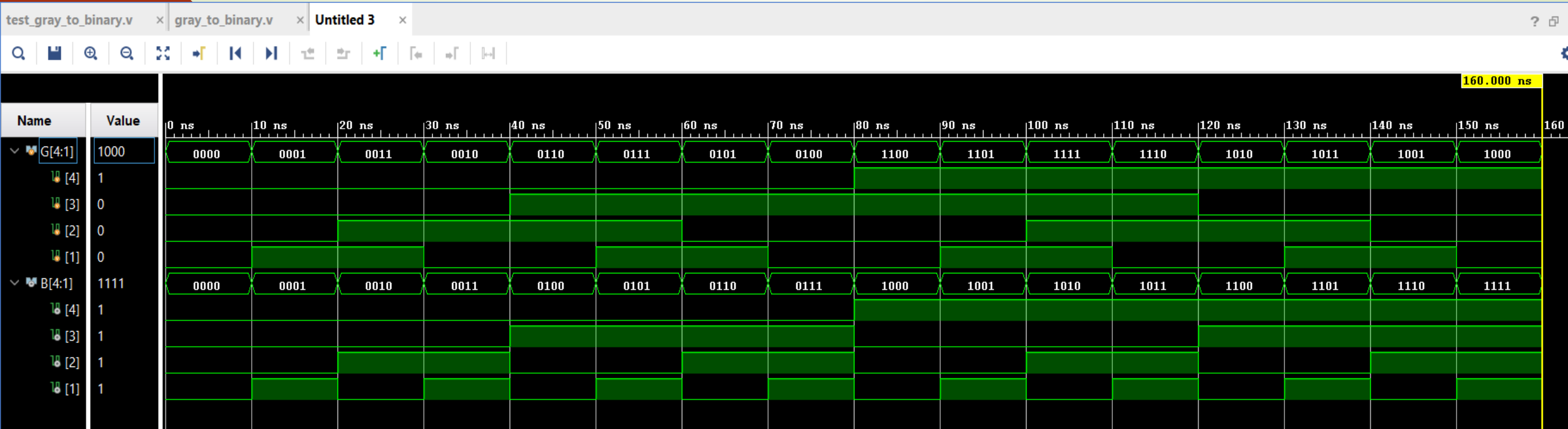
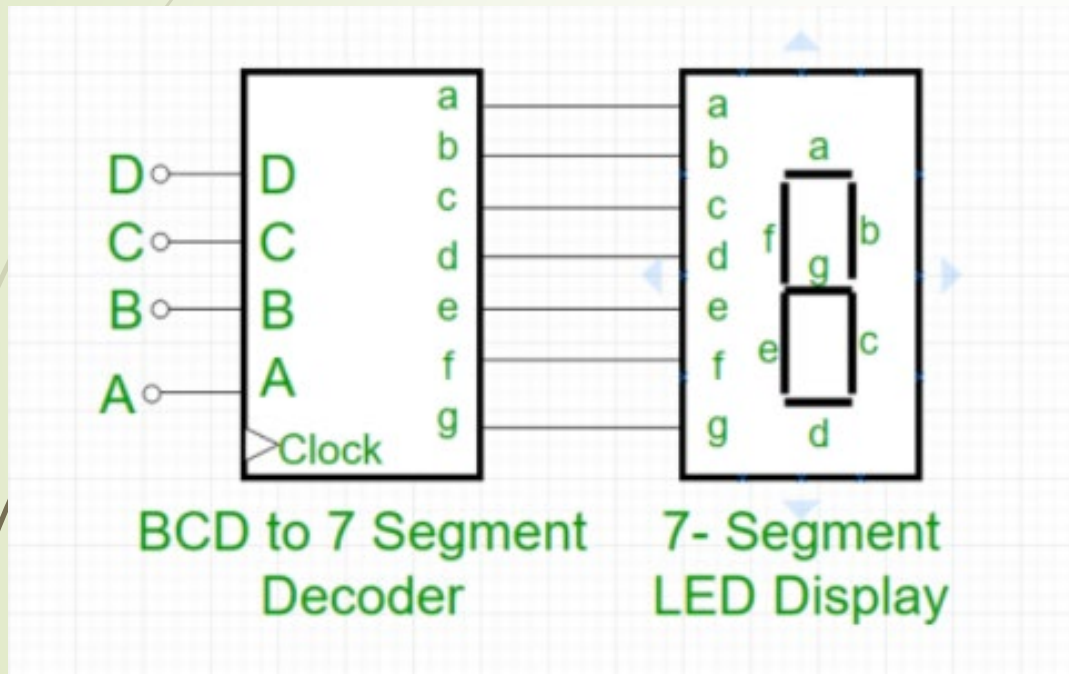
## Work 2 : BCD to Seven Segment Display Decoder



Inputs				Segments							
A	B	C	D	a	b	c	d	e	f	g	
0	0	0	0	1	1	1	1	1	1	0	For display 0
0	0	0	1	0	1	1	0	0	0	0	For display 1
0	0	1	0	1	1	0	1	1	0	1	For display 2
0	0	1	1	1	1	1	1	0	0	1	For display 3
0	1	0	0	0	1	1	0	0	1	1	For display 4
0	1	0	1	1	0	1	1	0	1	1	For display 5
0	1	1	0	1	0	1	1	1	1	1	For display 6
0	1	1	1	1	1	1	0	0	0	0	For display 7
1	0	0	0	1	1	1	1	1	1	1	For display 8
1	0	0	1	1	1	1	1	0	1	1	For display 9
1	0	1	0	1	1	1	0	1	1	1	For display A
1	0	1	1	0	0	1	1	1	1	1	For display b
1	1	0	0	1	0	0	1	1	1	0	For display C
1	1	0	1	0	1	1	1	1	0	1	For display d
1	1	1	0	1	0	0	1	1	1	1	For display E
1	1	1	1	1	0	0	0	1	1	1	For display F

# CODE

```
test_seven_seg.v x seven_seg.v x Untitled 5 x
D:/YEAR 2/SEMESTER 2/DIGITAL DESIGN/LABS/LAB 2/seven_seg.v

1 | `timescale 1ns / 1ps
2 | ////////////////////////////////////////////
21 |
22 |
23 | module seven_seg(hex,led);
24 | input [3:0] hex;
25 | output [6:0] led;
26 | reg [6:0] led;
27 | always @(hex)
28 | begin
29 |     case (hex)
30 |         0 : led = 7'b1111110;
31 |         1 : led = 7'b0110000;
32 |         2 : led = 7'b1101101;
33 |         3 : led = 7'b1111001;
34 |         4 : led = 7'b0110011;
35 |         5 : led = 7'b1011011;
36 |         6 : led = 7'b1011111;
37 |         7 : led = 7'b1110000;
38 |         8 : led = 7'b1111111;
39 |         9 : led = 7'b1111011;
40 |         10 : led = 7'b1110111;
41 |         11 : led = 7'b0011111;
42 |         12 : led = 7'b1001110;
43 |         13 : led = 7'b0111101;
44 |         14 : led = 7'b1001111;
45 |         15 : led = 7'b1000111;
46 |         default : led = 7'b1111111;
47 |     endcase
48 | end
49 |
50 | endmodule
```

```
module seven_seg(hex,led);
input [3:0] hex;
output [6:0] led;
reg [6:0] led;
always @(hex)
begin
    case (hex)
        0 : led = 7'b1111110;
        1 : led = 7'b0110000;
        2 : led = 7'b1101101;
        3 : led = 7'b1111001;
        4 : led = 7'b0110011;
        5 : led = 7'b1011011;
        6 : led = 7'b1011111;
        7 : led = 7'b1110000;
        8 : led = 7'b1111111;
        9 : led = 7'b1111011;
        10 : led = 7'b1110111;
        11 : led = 7'b0011111;
        12 : led = 7'b1001110;
        13 : led = 7'b0111101;
        14 : led = 7'b1001111;
        15 : led = 7'b1000111;
        default : led = 7'b1111111;
    endcase
end

endmodule
```

# TEST BENCH

Project Summary x test\_seven\_seg.v x

D:/YEAR 2/SEMESTER 2/DIGITAL DESIGN/LABS/LAB 2/test\_seven\_seg.v



Q [Icons]

```
1  `timescale 1ns / 1ps
2  //////////////////////////////////////////
21
22
23  module test_seven_seg;
24      reg [3:0] hex;
25      wire [6:0] led;
26      seven_seg S1(hex,led);
27
28  initial
29  begin
30      hex = 0;
31      #10 hex = 1;
32      #10 hex = 2;
33      #10 hex = 3;
34      #10 hex = 4;
35      #10 hex = 5;
36      #10 hex = 6;
37      #10 hex = 7;
38      #10 hex = 8;
39      #10 hex = 9;
40      #10 hex = 10;
41      #10 hex = 11;
42      #10 hex = 12;
43      #10 hex = 13;
44      #10 hex = 14;
45      #10 hex = 15;
46  end
47
48  initial #160 $finish;
49  endmodule
```

```
module test_seven_seg;
reg [3:0] hex;
wire [6:0] led;
seven_seg S1(hex,led);
```

```
initial
begin
    hex = 0;
    #10 hex = 1;
    #10 hex = 2;
    #10 hex = 3;
    #10 hex = 4;
    #10 hex = 5;
    #10 hex = 6;
    #10 hex = 7;
    #10 hex = 8;
    #10 hex = 9;
    #10 hex = 10;
    #10 hex = 11;
    #10 hex = 12;
    #10 hex = 13;
    #10 hex = 14;
    #10 hex = 15;
end
```

```
initial #160 $finish;
endmodule
```

 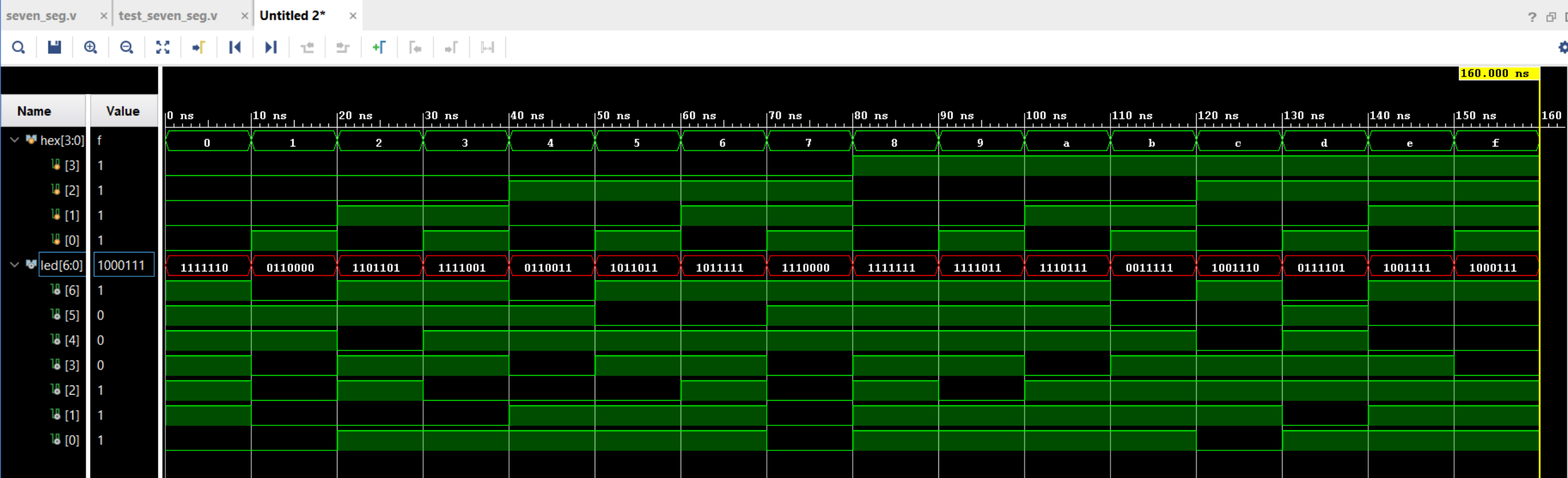

SIMULATION

# Work 3

Implement a Buzzer system in Verilog. Write test bench and verify various cases.


- There are 2 participant with a push button each.- Indicate when to press the button. (This is the host control)
- Indicate who is pressing the button first (who wins the chance)
- Disable the button of the other participant.

INPUT			OUTPUT	
a	b	control	A	B
0	0	0	X	X
0	0	1	0	0
0	1	0	X	X
1	0	0	X	X
0	1	1	Z	1
1	0	1	1	Z
1	1	1	Z	Z

TRUTH  
TABLE



TRI STATE  
BUFFER

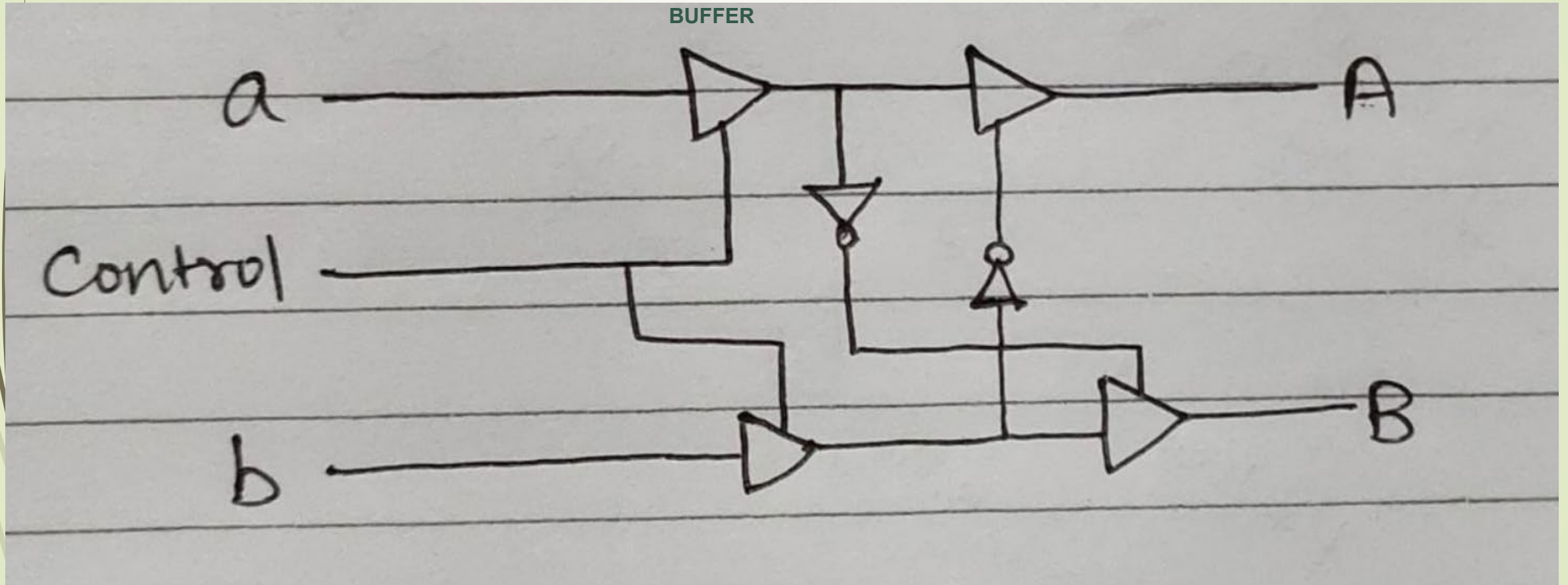

CIRCUIT DIAGRAM

D:/YEAR 2/SEMESTER 2/DIGITAL DESIGN/LABS/LAB 2/Two\_Player\_Buzzer.v



```
1  `timescale 1ns / 1ps
2  ///////////////////////////////////////////////////
3  // Company:
4  // Engineer:
5  //
6  // Create Date: 20.01.2022 19:26:39
7  // Design Name:
8  // Module Name: Two_Player_Buzzer
9  // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////
21
22 module Two_Player_Buzzer(a,b,control,A,B);
23   input a,b,control;
24   output A,B;
25   wire p,q;
26
27   assign p = control ? a : 'bz;
28   assign q = control ? b : 'bz;
29   assign A= ~q ? p : 'bz;
30   assign B= ~p ? q : 'bz;
31
32 endmodule
```

# CODE

```
module Two_Player_Buzzer(a,b,control,A,B);
input a,b,control;
output A,B;
wire p,q;
```

```
assign p = control ? a : 'bz;
assign q = control ? b : 'bz;
assign A= ~q ? p : 'bz;
assign B= ~p ? q : 'bz;
```

```
endmodule
```



# TEST BENCH

Project Summary x Two\_Player\_Buzzer.v x Test\_Bench\_Two\_Player\_Buzzer.v x

D:/YEAR 2/SEMESTER 2/DIGITAL DESIGN/LABS/LAB 2/Test\_Bench\_Two\_Player\_Buzzer.v

```
1  `timescale 1ns / 1ps
2  //////////////////////////////////////
21
22
23  module Test_Bench_Two_Player_Buzzer;
24
25      wire A,B;
26      reg a,b,control;
27
28      Two_Player_Buzzer G(a,b,control,A,B);
29  initial
30  begin
31
32      a = 1'b0; b = 1'b0; control = 1'b0;
33      #10;
34      a = 1'b0; b = 1'b0; control = 1'b1;
35      #10;
36      a = 1'b0; b = 1'b1; control = 1'b0;
37      #10;
38      a = 1'b1; b = 1'b0; control = 1'b0;
39      #10;
40      a = 1'b0; b = 1'b1; control = 1'b1;
41      #10;
42      a = 1'b1; b = 1'b0; control = 1'b1;
43      #10;
44      a = 1'b1; b = 1'b1; control = 1'b1;
45      #10;
46  end
47  initial #80 $finish;
48  endmodule
```

```
module Test_Bench_Two_Player_Buzzer;


wire A,B;
reg a,b,control;

Two_Player_Buzzer G(a,b,control,A,B);
initial
begin

 
a = 1'b0; b = 1'b0; control = 1'b0;
#10;
a = 1'b0; b = 1'b0; control = 1'b1;
#10;
a = 1'b0; b = 1'b1; control = 1'b0;
#10;
a = 1'b1; b = 1'b0; control = 1'b0;
#10;
a = 1'b0; b = 1'b1; control = 1'b1;
#10;
a = 1'b1; b = 1'b0; control = 1'b1;
#10;
a = 1'b1; b = 1'b1; control = 1'b1;
#10;
end
initial #80 $finish;
endmodule
```









 





















Two\_Player\_Buzzer.v × Test\_Bench\_Two\_Player\_Buzzer.v × **Untitled 2** ×





# SIMULATION



Name	Value	Name	Value	Name	Value	Name	Value	Name	Value	Name	Value
 A	X	 A	0	 A	X	 A	X	 A	Z	 A	1
 B	X	 B	0	 B	X	 B	X	 B	1	 B	Z
 a	0	 a	0	 a	0	 a	1	 a	0	 a	1
 b	0	 b	0	 b	1	 b	0	 b	1	 b	0
 control	0	 control	1	 control	0	 control	0	 control	1	 control	1



**THANK YOU**